


Inductance



Mutual Inductance

Interaction between two loops :

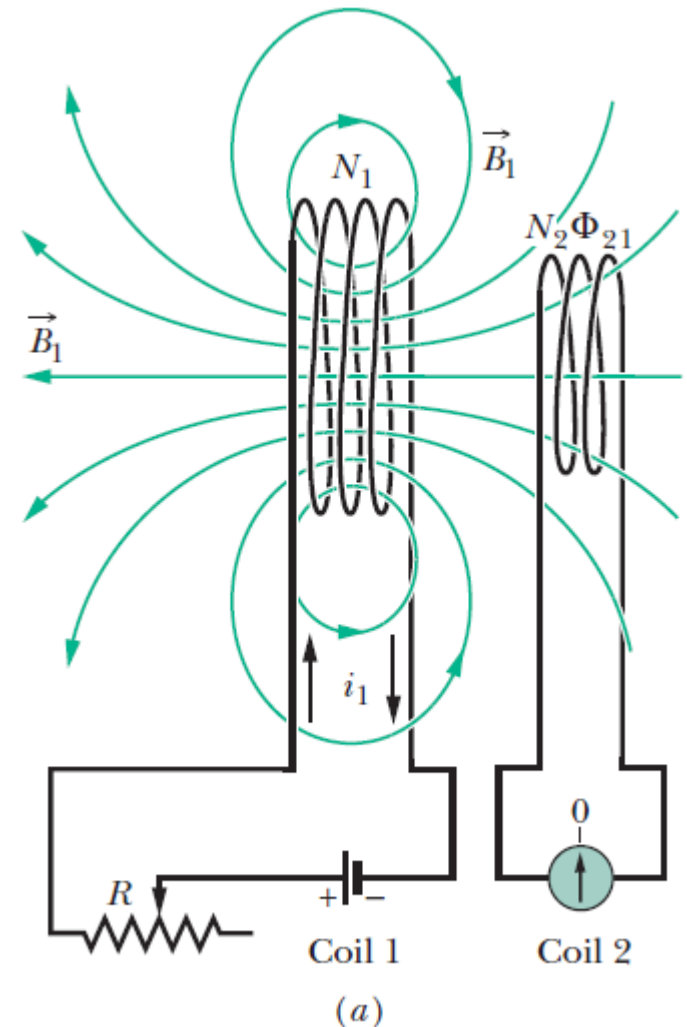
- The magnetic field $\mathbf{B}_1$, produced by current I_1 in coil 1 extends through coil 2.
- If I_1 is varied, *an emf is induced in coil 2* and current registers on the meter connected to coil 2.



Mutual Inductance

Interaction between two loops :

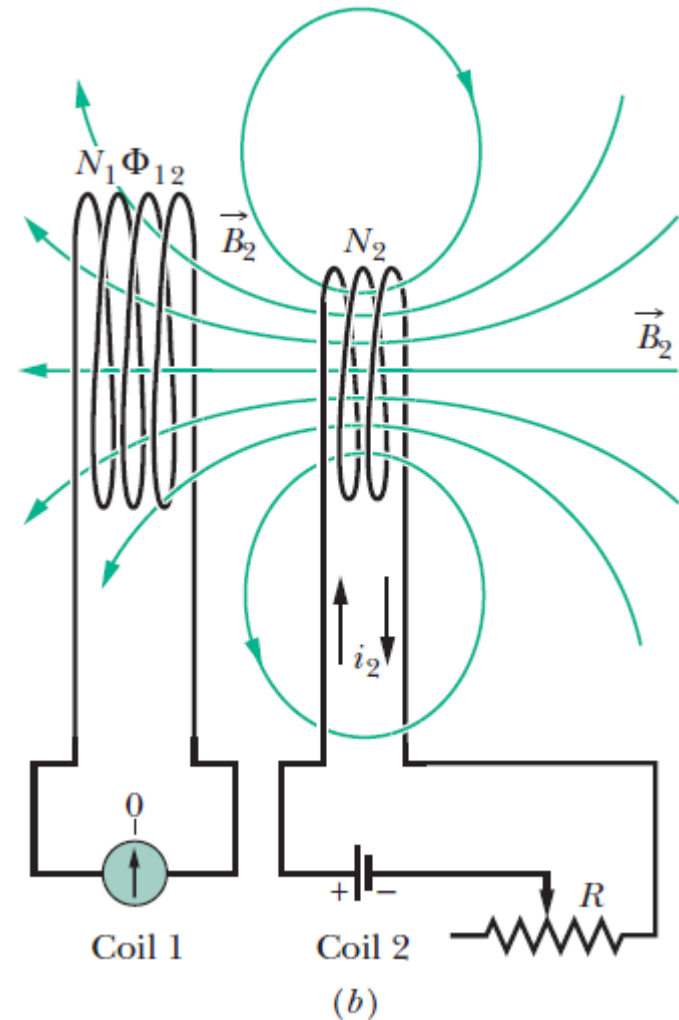- The roles of the coils interchanged:
The magnetic field $\mathbf{B}_2$, produced by current I_2 in coil 2 extends through coil 1.
- If I_2 is varied, *an emf is induced in coil 1*.



Mutual Inductance

Interaction between two loops :

- The field produced by coil (1):*


$$\vec{B} = k_m \int \frac{I d\vec{L} \times \vec{r}}{r^3}$$

- The **flux** of the field B_1 through the second coil (2):

$$\Phi_2 = \iint \vec{B}_1 \cdot d\vec{A}_2$$

$$= M_{21} I_1$$

$$M_{21} = \text{Mutual inductance}$$

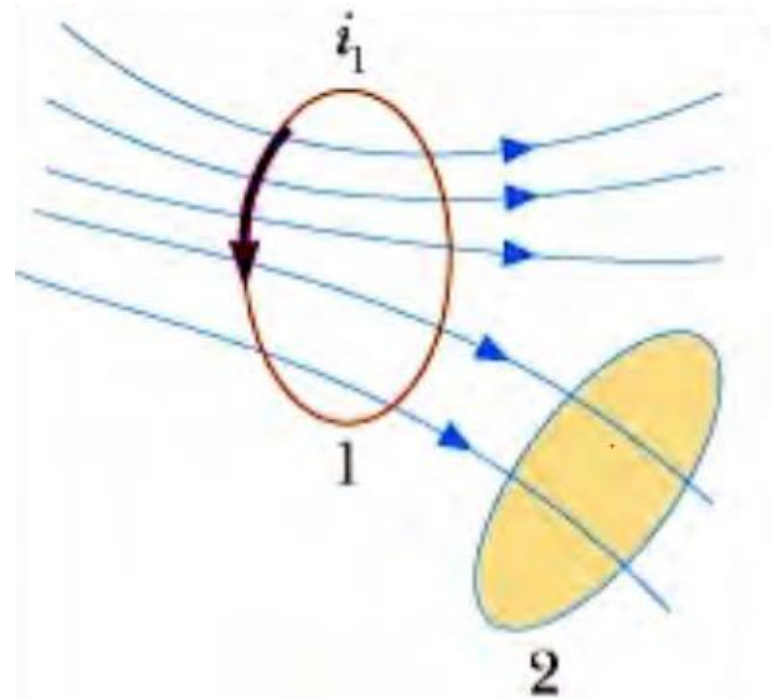

Mutual Inductance


Interaction between two loops :

- *Flux of the field B_2 through the first coil (1) :*

$$\Phi_1 = M_{12} I_2$$

- *The quantities M_{12} , M_{21} are determined by the geometry of the setup:*

$$M_{21} = M_{12} = M$$

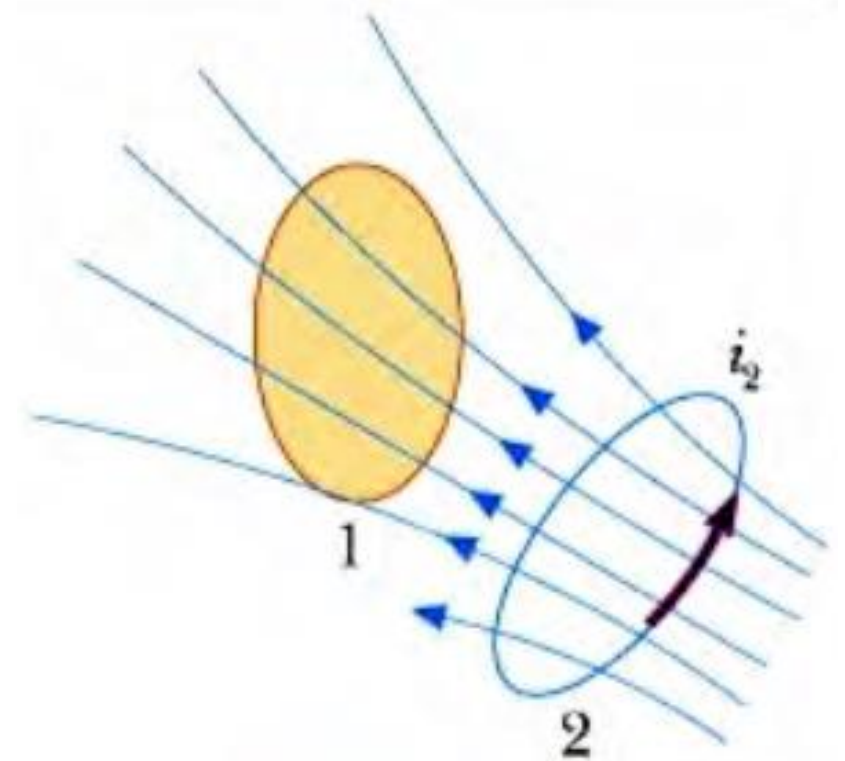

Mutual Inductance

The Mutual Inductance:

- The total flux through each coil :*


$$N_1 \Phi_1 = M I_2$$

$$N_2 \Phi_2 = M I_1$$

- The mutual inductance M :*

$$M = \frac{N_1 \Phi_1}{I_2} = \frac{N_2 \Phi_2}{I_1}$$

Units: Weber/Ampere = Henry

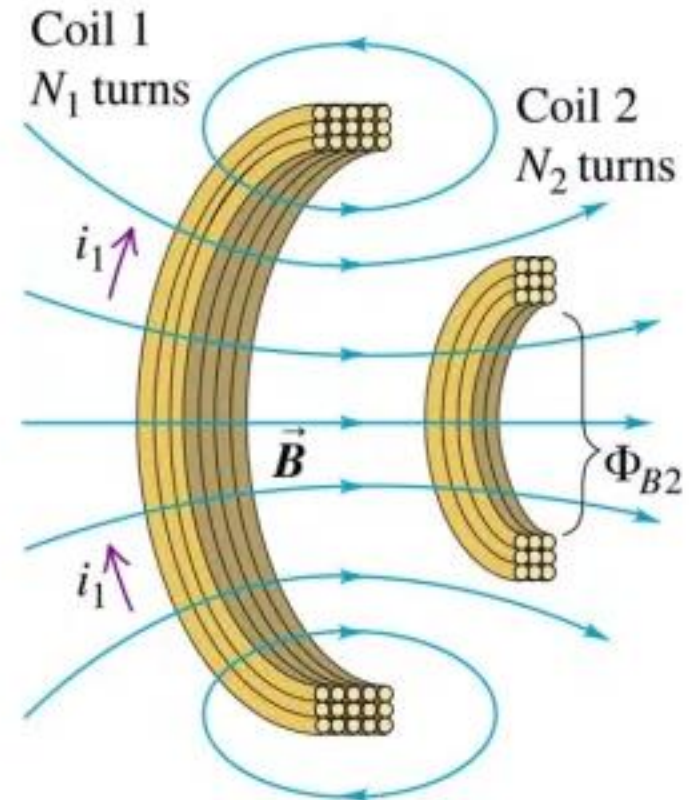

Mutual Inductance

The Mutual Inductance:


When the current in one coil changes:

- The induced emf in the other coil :*

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_2}{dt} = -M \frac{dI_1}{dt}$$

- Likewise:*


$$\mathcal{E}_1 = -M \frac{dI_2}{dt}$$

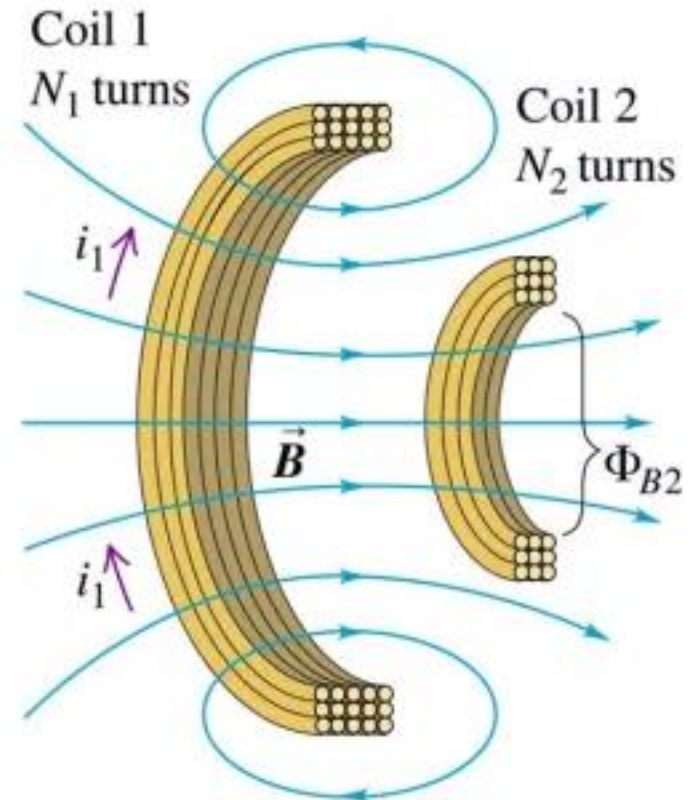

Mutual Inductance

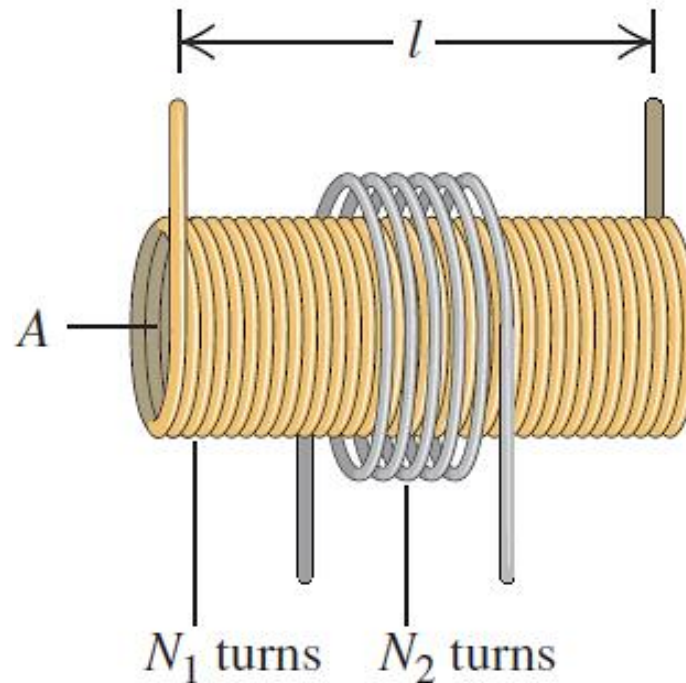Example: Calculating mutual inductance

In one form of a *Tesla coil*, a long solenoid with length ℓ and cross-sectional area A is closely wound with N_1 turns of wire. A coil with N_2 turns surrounds it at its center. Find the mutual inductance M .



Mutual Inductance

Example: Calculating mutual inductance

Solution:

$$B_1 = \mu_0 n_1 i_1 = \frac{\mu_0 N_1 i_1}{l}$$

$$M = \frac{N_2 \Phi_{B2}}{i_1} = \frac{N_2 B_1 A}{i_1} = \frac{N_2 \mu_0 N_1 i_1}{i_1 l} A = \frac{\mu_0 A N_1 N_2}{l}$$

For: $\ell=0.50$ m; $A=0.001$ m²; $N_1=1000$ turns; $N_2=10$ turns

$$\begin{aligned} M &= \frac{(4\pi \times 10^{-7} \text{ Wb/A} \cdot \text{m})(1.0 \times 10^{-3} \text{ m}^2)(1000)(10)}{0.50 \text{ m}} \\ &= 25 \times 10^{-6} \text{ Wb/A} = 25 \times 10^{-6} \text{ H} = 25 \text{ } \mu\text{H} \end{aligned}$$

Self-Inductance and Inductors

Self-inductance :

For a single isolated coil:


- The coil's *own magnetic field* causes a magnetic flux through the same coil.
- The total “self” flux:

$$N\Phi_m = L I$$

- The self-induced emf:

$$\mathcal{E}_1 = -L \frac{dI}{dt}$$

$$L = \text{Self-inductance}$$

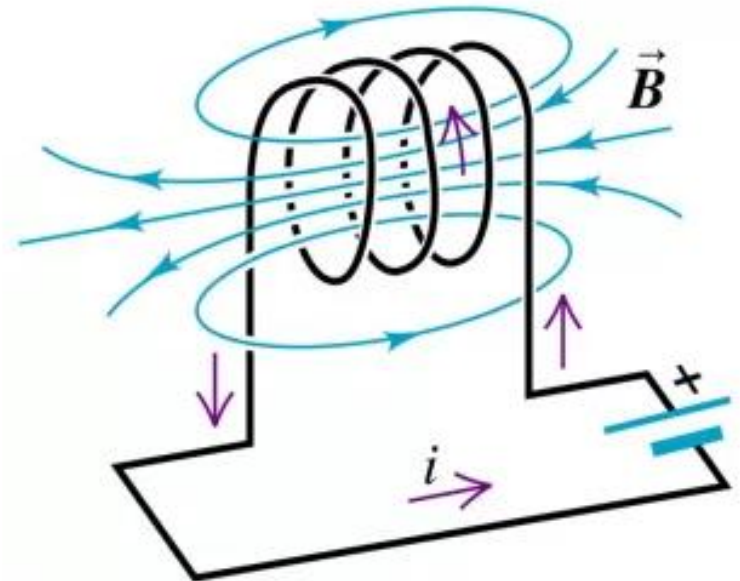

Self-Inductance and Inductors

Example: Ideal solenoid

Self-inductance of a solenoid of radius a with $n = N/\ell$ turns per unit length.

- *Field of solenoid:*



$$B = \mu_0 n I$$

- *Flux through one turn:*

$$\Phi_1 = (\mu_0 n I)(\pi a^2)$$

- *Self-inductance:*
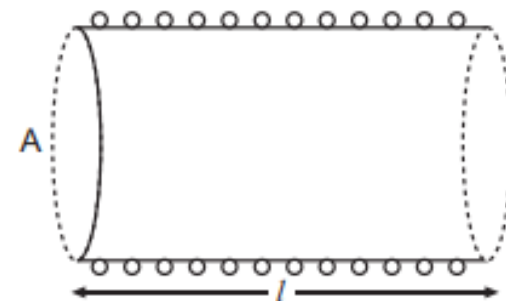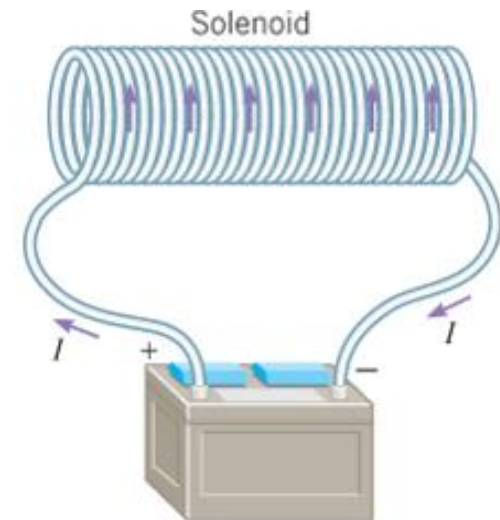
$$L = \frac{N\Phi_1}{I} = \mu_0 n^2 \ell (\pi a^2)$$



Self-Inductance and Inductors


Example:

Given: $n = 200$ turns/m; $A = 5.0 \text{ cm}^2$

$$\begin{aligned} L &= (4\pi \times 10^{-7})(200)^2(5.0 \times 10^{-4})\ell \\ &= (2.5 \times 10^{-5})\ell \end{aligned}$$

- Inductance per unit length:*
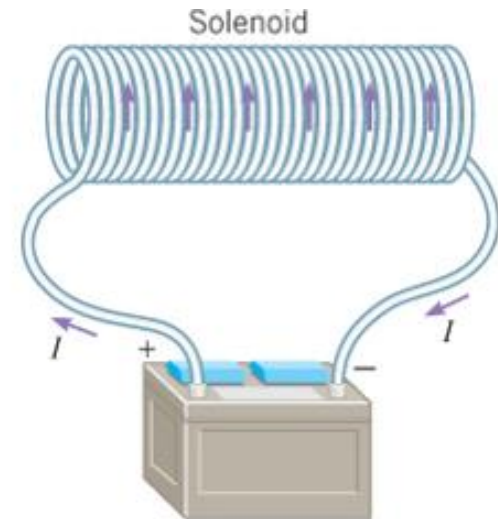
$$L/\ell = 2.5 \times 10^{-5} \text{ H/m}$$



Self-Inductance and Inductors


Inductors as Circuit Element:

- Self-induced emf (voltage):

$$\mathcal{E}_1 = -L \frac{dI}{dt}$$

- Voltage drop:
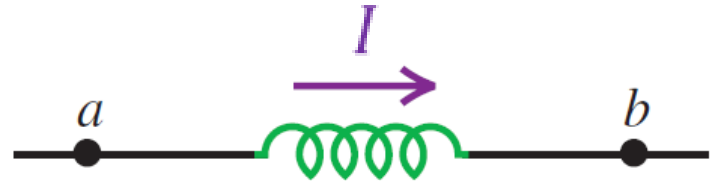
$$\begin{aligned} V_{ab} &= V_a - V_b \\ &= L \frac{dI}{dt} \end{aligned}$$




Self-Inductance and Inductors



Inductors as Circuit Element:

- When current I changes:

$$V_{ab} = L \frac{dI}{dt}$$

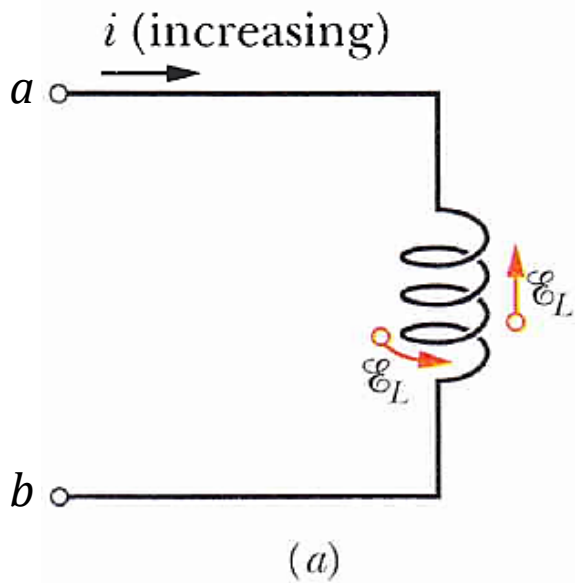

$$V_{ab} > 0$$

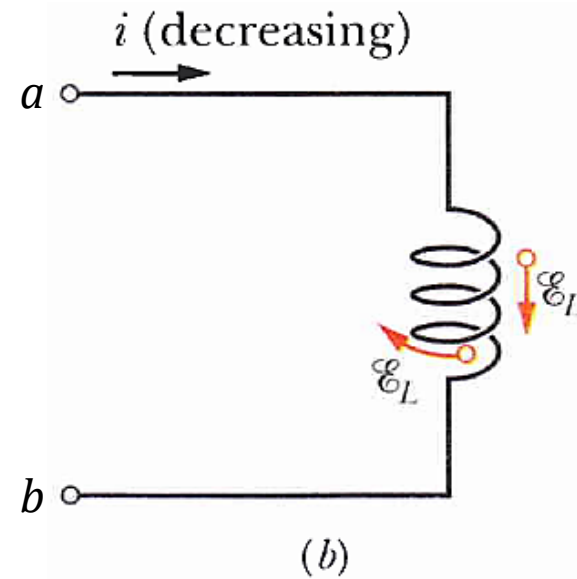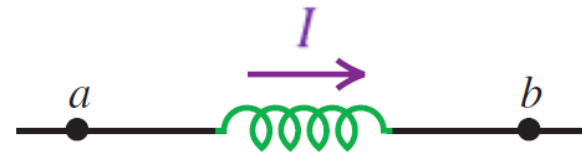


$$V_{ab} < 0$$

Self-Inductance and Inductors

Inductors as Circuit Element:


- Voltage for a resistor :*

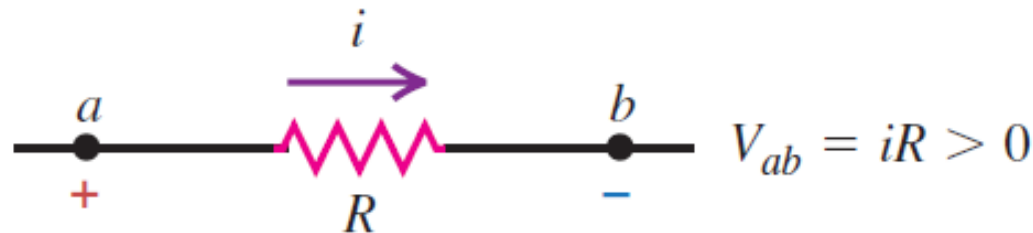(a) Resistor with current i flowing from a to b :
potential drops from a to b .



- Voltage for an inductor:*

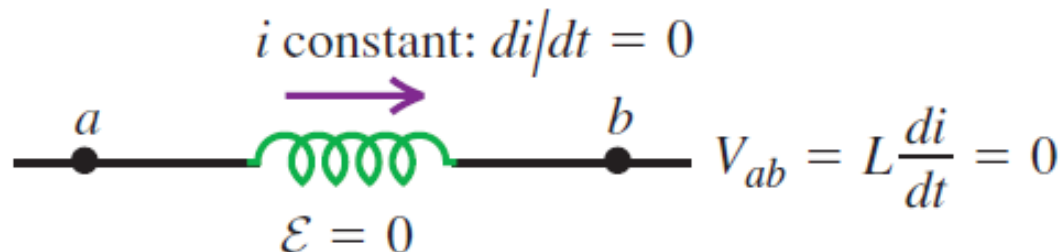(b) Inductor with *constant* current i flowing
from a to b : no potential difference.




Self-Inductance and Inductors


Inductors as Circuit Element:

- Voltage for an inductor:

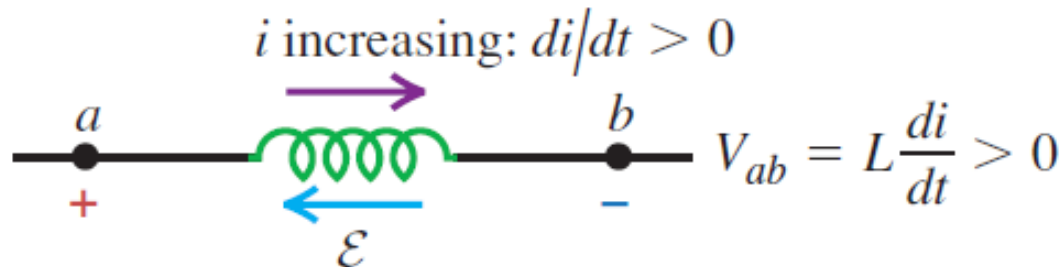(c) Inductor with *increasing* current i flowing from a to b : potential drops from a to b .



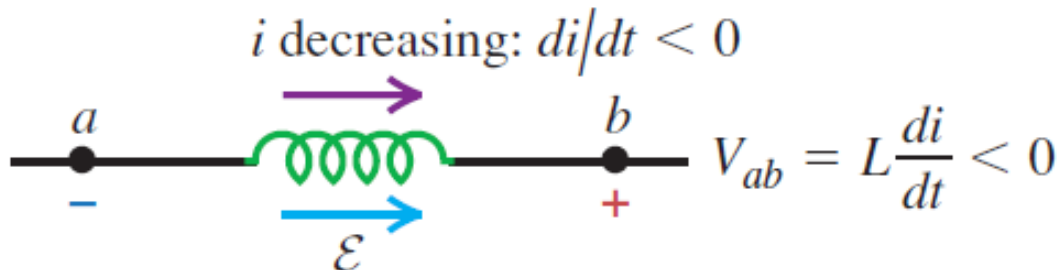(d) Inductor with *decreasing* current i flowing from a to b : potential increases from a to b .



Self-Inductance and Inductors

Example:

If the current in the solenoid of $L=40\text{ }\mu\text{H}$ increases uniformly from 0 to 6.0 A in 3.0 μs , find the magnitude and direction of the self-induced emf.

Solution:

$$\frac{dI}{dt} = \frac{6.0\text{ A}}{3.0 \times 10^{-6}\text{ s}} = 2.0 \times 10^6\text{ A/s}$$

- *Inductor voltage:*

$$\begin{aligned} V_{ab} &= L \frac{dI}{dt} \\ &= (40 \times 10^{-6}\text{ H})(2.0 \times 10^6\text{ As}) = 80\text{ V} \end{aligned}$$

Magnetic-Field Energy

Energy Stored in an Inductor

- *Electrical power:*

$$P = \frac{dU}{dt} = IV_{ab} = L I \frac{dI}{dt}$$

- *Total energy needed to set the current to I_f :*

$$\begin{aligned} U &= \int P dt = L \int_0^{I_f} I dI \\ &= \frac{1}{2} L I_f^2 \end{aligned}$$

*Energy **stored** in the inductor.*

Magnetic-Field Energy

Example: Ideal solenoid

- *Field and inductance:*

$$B = \mu_0 n I \quad L = \mu_0 n^2 (\ell A)$$

- *Energy stored:*

$$\begin{aligned} U &= \frac{1}{2} L I^2 = \frac{1}{2} (\mu_0 n^2 \ell A) I^2 \\ &= \frac{1}{2} \frac{1}{\mu_0} (\mu_0^2 n^2 I^2) (\ell A) \end{aligned}$$

- *Energy density:*

$$u = \frac{U}{(\ell A)} = \frac{B^2}{2\mu_0}$$

*Energy **stored** in the inductor.*


R-L Circuits

Series circuit:

$$\mathcal{E}_0 - V_R - V_L = 0$$

$$\mathcal{E}_0 - IR - L \frac{dI}{dt} = 0$$

$$L \frac{dI}{dt} + IR = \mathcal{E}_0$$

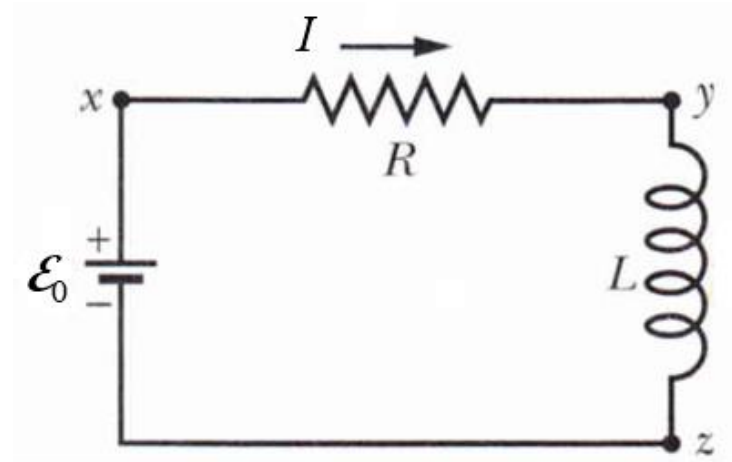

- Solution:

$$I(t) = \frac{\mathcal{E}_0}{R} + ce^{-(R/L)t}$$

- Given $I = 0$ at $t = 0$:

$$I(t) = \frac{\mathcal{E}_0}{R} [1 - e^{-(R/L)t}]$$

R-L Circuits



Series circuit:

$$I(t) = \frac{\mathcal{E}_0}{R} [1 - e^{-(R/L)t}]$$

$$I(t) = \frac{\mathcal{E}_0}{R} [1 - e^{-(t/\tau)}]$$

- The time constant τ :

$$\tau = R/L$$

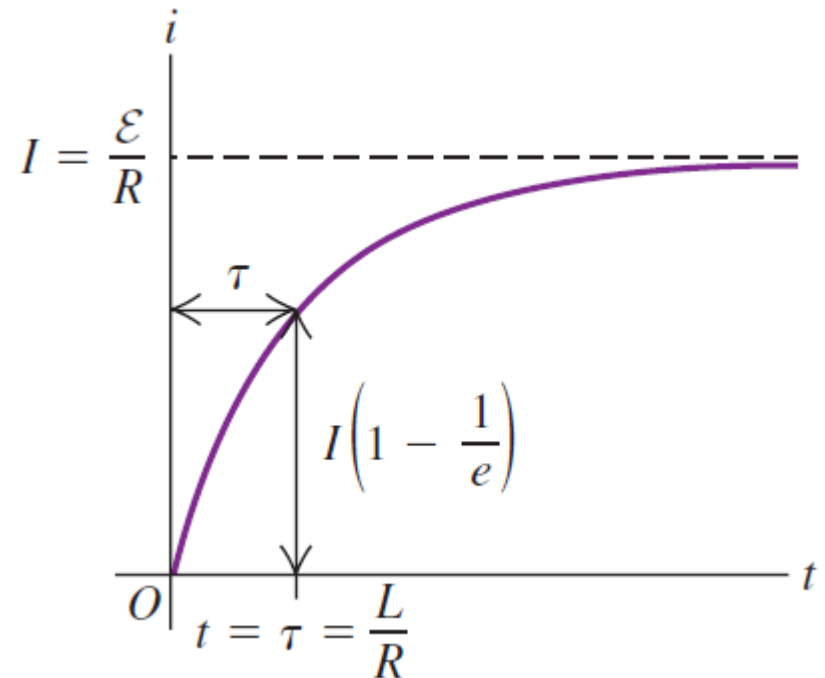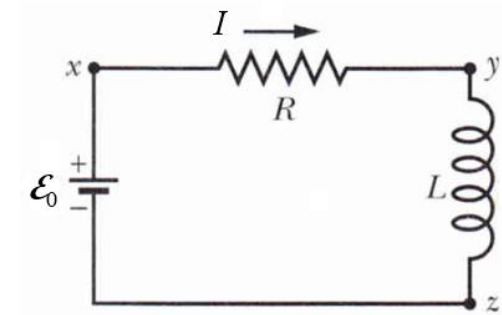

R-L Circuits


Series circuit:

Example:

$$\mathcal{E}_0 = 10 \text{ V} ; R = 2 \text{ k}\Omega ; L = 4.0 \text{ H}$$

$$\tau = 2 \text{ ms}$$
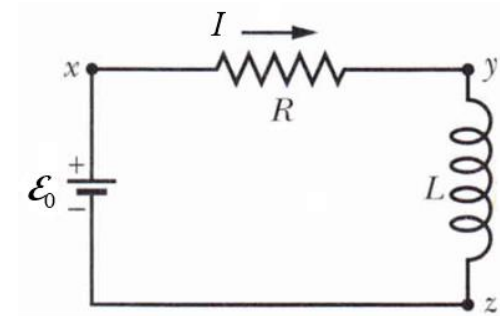
$$I(t) = (5 \times 10^{-3})[1 - e^{500t}] \text{ A}$$



- The voltages:

$$V_R = IR = 10.0 [1 - e^{500t}] \text{ V}$$

$$V_L = L(dI/dt) = 10.0 e^{500t} \text{ V}$$

R-L Circuits

Series circuit:



Example:

$$\mathcal{E}_0 = 10 \text{ V} ; R = 2 \text{ k}\Omega ; L = 4.0 \text{ H}$$

- The voltages:

$$V_R = 10.0 [1 - e^{500t}] \text{ V}$$



$$V_L = 10.0 e^{500t} \text{ V}$$

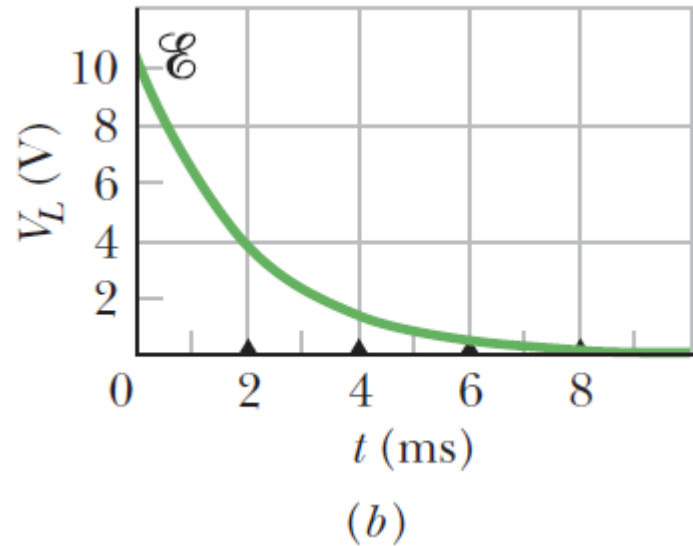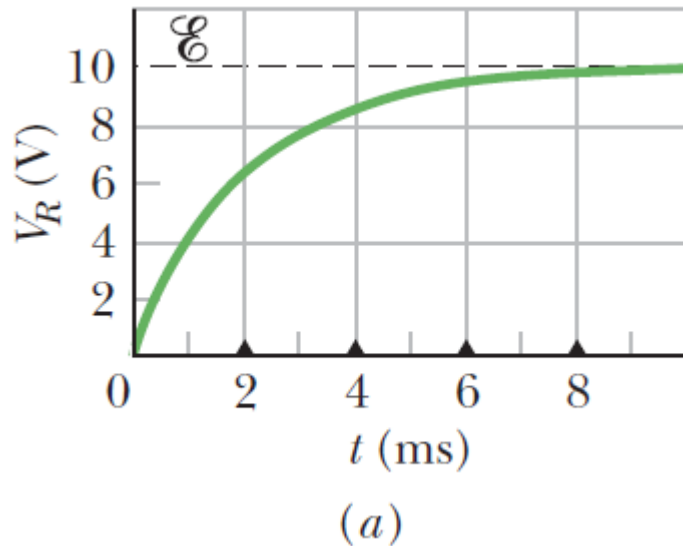

R-L Circuits

Series circuit – current decay:

Circuit with two-way switch :

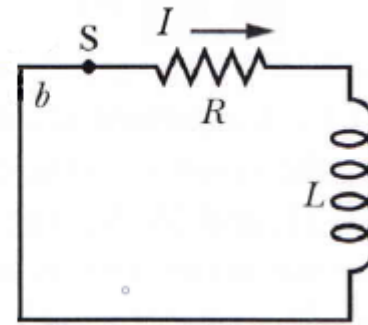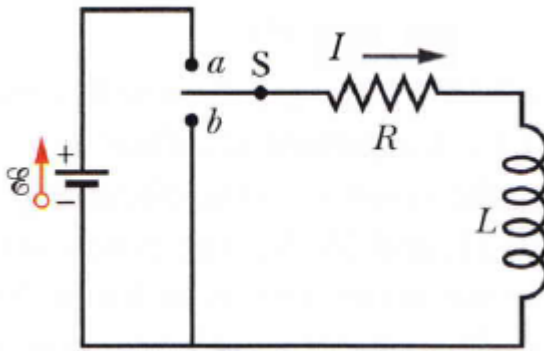


- *Switch at position b:*

$$L \frac{dI}{dt} + IR = 0$$

- *Solution:*

$$I(t) = I_0 e^{-(RL)t}$$

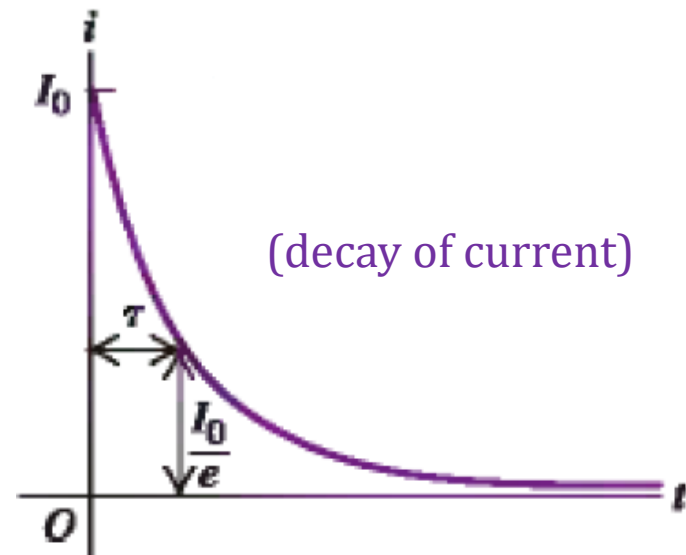

L-C Circuits

LC Series circuit:

When an initially charged capacitor C is connected to an inductor L .

- *At $t=0$ circuit is switched to the right.*



$$V_C = V_L$$

$$\frac{q}{C} = L \frac{dI}{dt}$$

- *But*

$$I = -\frac{dq}{dt}$$

(the current discharges the capacitor)

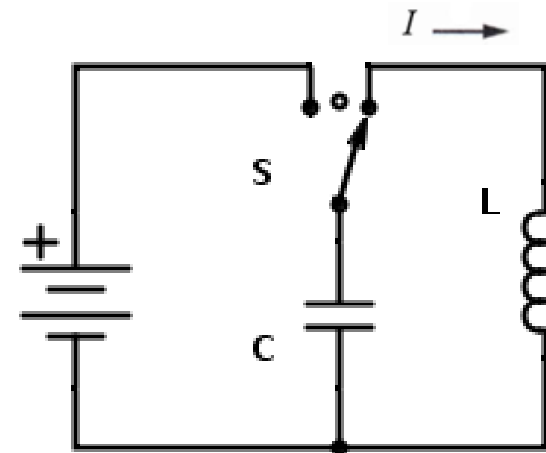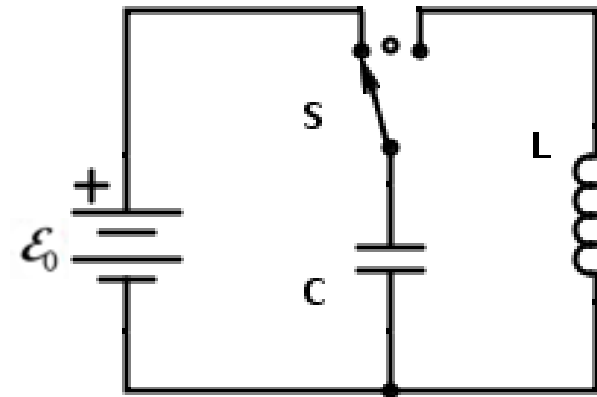


L-C Circuits

Series circuit:

When an initially charged capacitor C is connected to an inductor L .
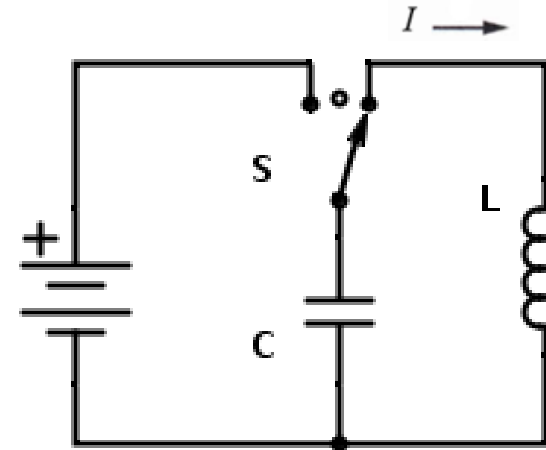
$$\frac{q}{C} = -L \frac{d^2 q}{dt^2}$$
$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$



Simple harmonic oscillator equation

- *Solution*

$$q(t) = Q \cos(\omega t + \phi) \quad \text{where} \quad \omega = \frac{1}{\sqrt{LC}}$$

(Q , ϕ = constants to be determined)

L-C Circuits

Series circuit:

When an initially charged capacitor C is connected to an inductor L .


$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$

- Solution*

$$q(t) = Q \cos(\omega t + \phi)$$

$$I(t) = \omega Q \sin(\omega t + \phi)$$
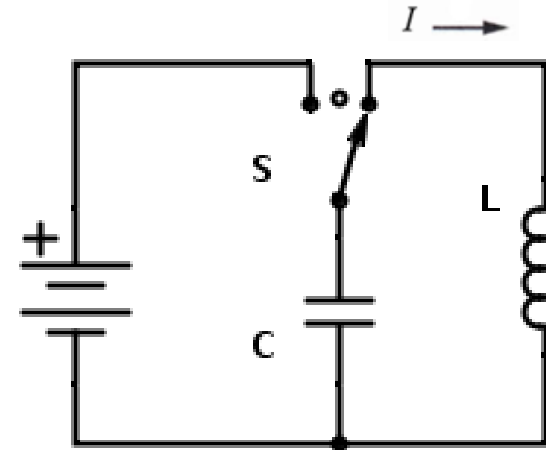
$$\text{where } \omega = \frac{1}{\sqrt{LC}}$$



L-C Circuits

Example:

A 300-V power supply is used to charge a 25- μ F capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a 10-mH inductor. a) Find the angular frequency ω ; and b) Find the capacitor charge at $t = 1.2$ ms.

- *Given*

$$\omega = \frac{1}{\sqrt{LC}} = 2 \times 10^3 \text{ rad/s}$$

$$Q_0 = CV_0 = 7.5 \times 10^{-3} \text{ C}$$

$$q(t) = Q \cos(\omega t + \phi)$$

$$I(t) = \omega Q \sin(\omega t + \phi)$$

$$(f = \omega/2\pi = 320 \text{ Hz} \quad T = 1/f = 3.1 \text{ ms})$$

L-C Circuits

Example:

- *Initial conditions:* At $t = 0$: $Q = Q_0$ $I = 0$

$$q(t) = (0.0075 \text{ C})\cos(2000t) \quad I(t) = (15 \text{ A})\sin(2000t)$$


- At $t = 1.2 \times 10^{-3} \text{ s}$

$$q(0.0012 \text{ s}) = -5.5 \times 10^{-3} \text{ C} \quad I(0.0012 \text{ s}) = 10 \text{ A}$$

L-C Circuits

Series circuit:
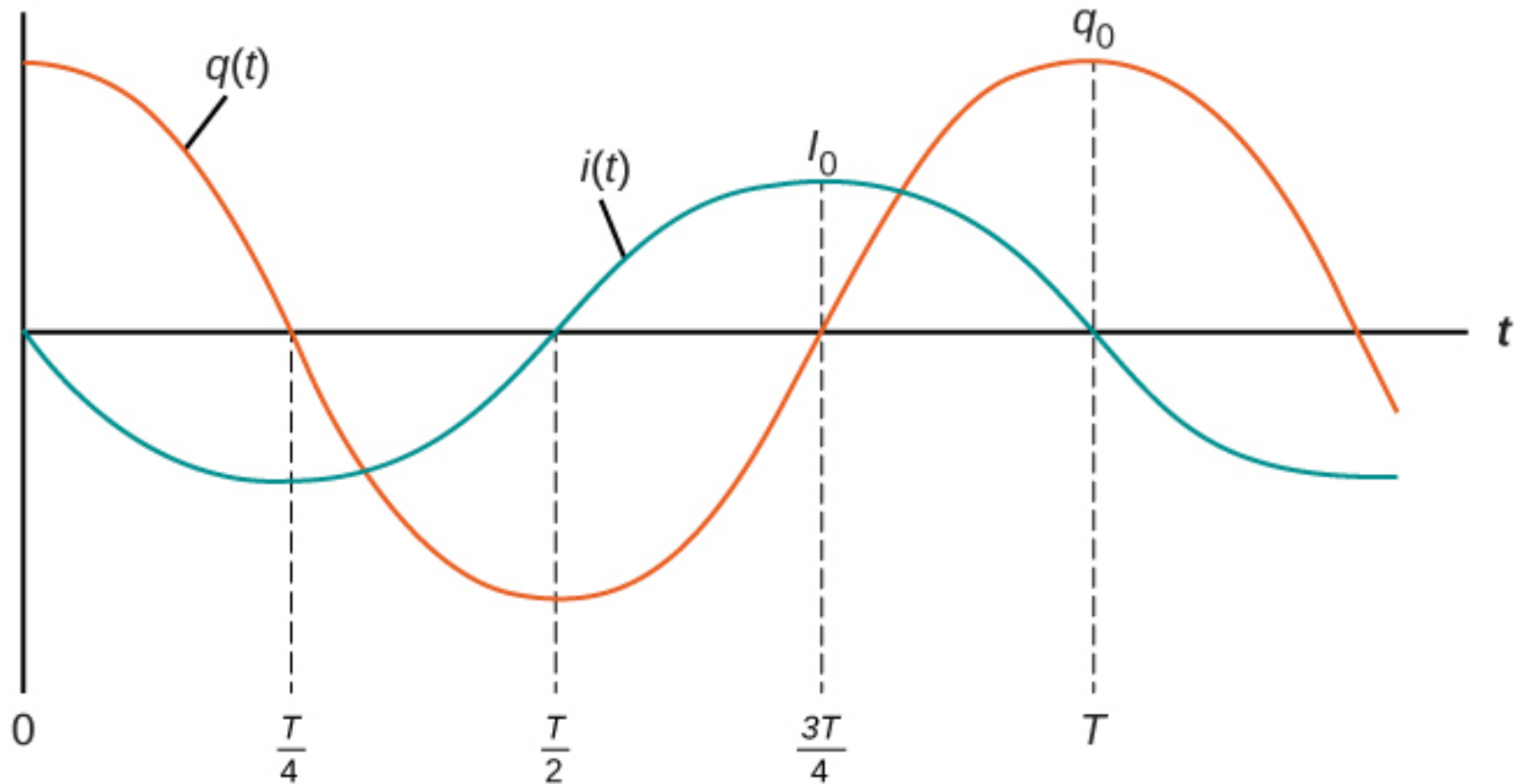
$$q(t) = Q_0 \cos(\omega t) \quad i(t) = -I_0 \sin(\omega t)$$



L-C Circuits

Series circuit: Electrical Energy

$$q(t) = Q_0 \cos(\omega t) \quad I(t) = I_0 \sin(\omega t)$$

- *Total electrical energy:*

$$U = U_C + U_L = \frac{1}{2C} q^2(t) + \frac{L}{2} I^2(t)$$

$$= \frac{Q_0^2}{2C} \cos^2(\omega t) + \frac{L I_0^2}{2} \sin^2(\omega t)$$

But: $I_0 = \omega Q_0$

$$U = \frac{1}{2} \frac{Q_0^2}{C} = \frac{1}{2} L I_0^2$$


Total energy is constant

L-C Circuits

Series circuit: Electrical Energy

- *Total electrical energy:*
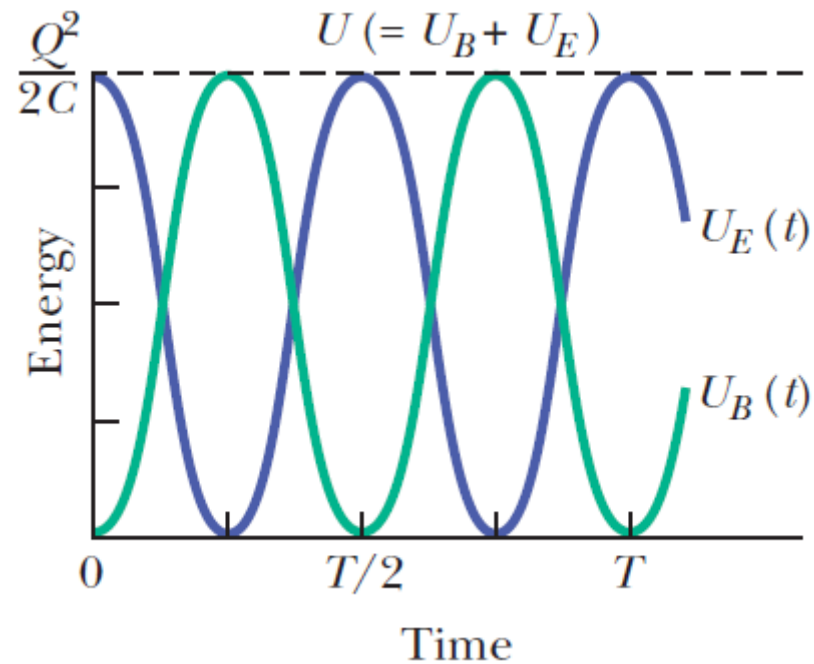
$$U = \frac{1}{2C} q^2(t) + \frac{L}{2} I^2(t)$$



The L-R-C Series Circuit

Charged capacitor C is connected to R and L:

- At $t=0$ circuit is switched to the right.*


$$V_C = V_L + V_R$$

$$\frac{q}{C} = L \frac{dI}{dt} + RI$$

- But $I = -(dq/dt)$*

$$\frac{q}{C} = -L \frac{d^2q}{dt^2} - R \frac{dq}{dt}$$
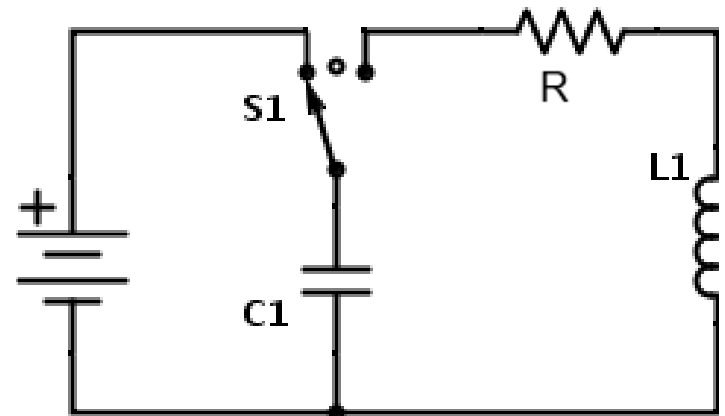
$$\frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{LC} q = 0$$



Damped harmonic oscillator equation

The L-R-C Series Circuit

Charged capacitor C is connected to R and L:

$$\frac{d^2q}{dt^2} + \left(\frac{R}{L}\right) \frac{dq}{dt} + \frac{q}{LC} = 0$$

- Let


$$\frac{1}{LC} = \omega_0^2 \quad \frac{R}{L} = 2\beta$$

$$\frac{d^2q}{dt^2} + 2\beta \frac{dq}{dt} + \omega_0^2 q = 0$$

- Solution

$$q(t) = Ae^{-\beta t} \cos(\omega_1 t + \phi) \quad \text{where} \quad \omega_1 = \sqrt{\omega_0^2 - \beta^2}$$
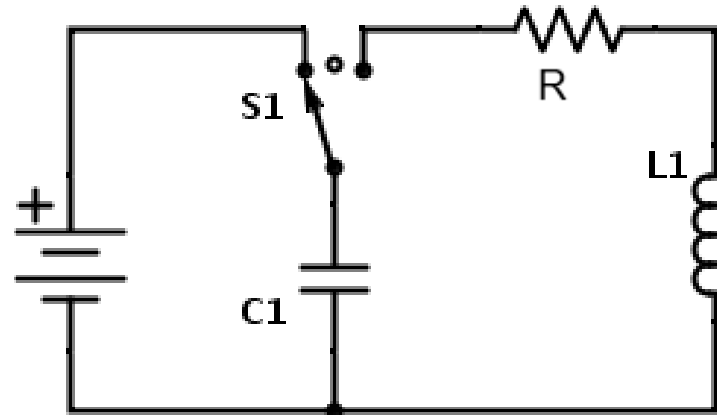
$$(Ae^{-\beta t}) = \text{decaying amplitude}$$



The L-R-C Series Circuit

Damped harmonic oscillation:

$$q(t) = Ae^{-\beta t} \cos(\omega_1 t + \phi)$$

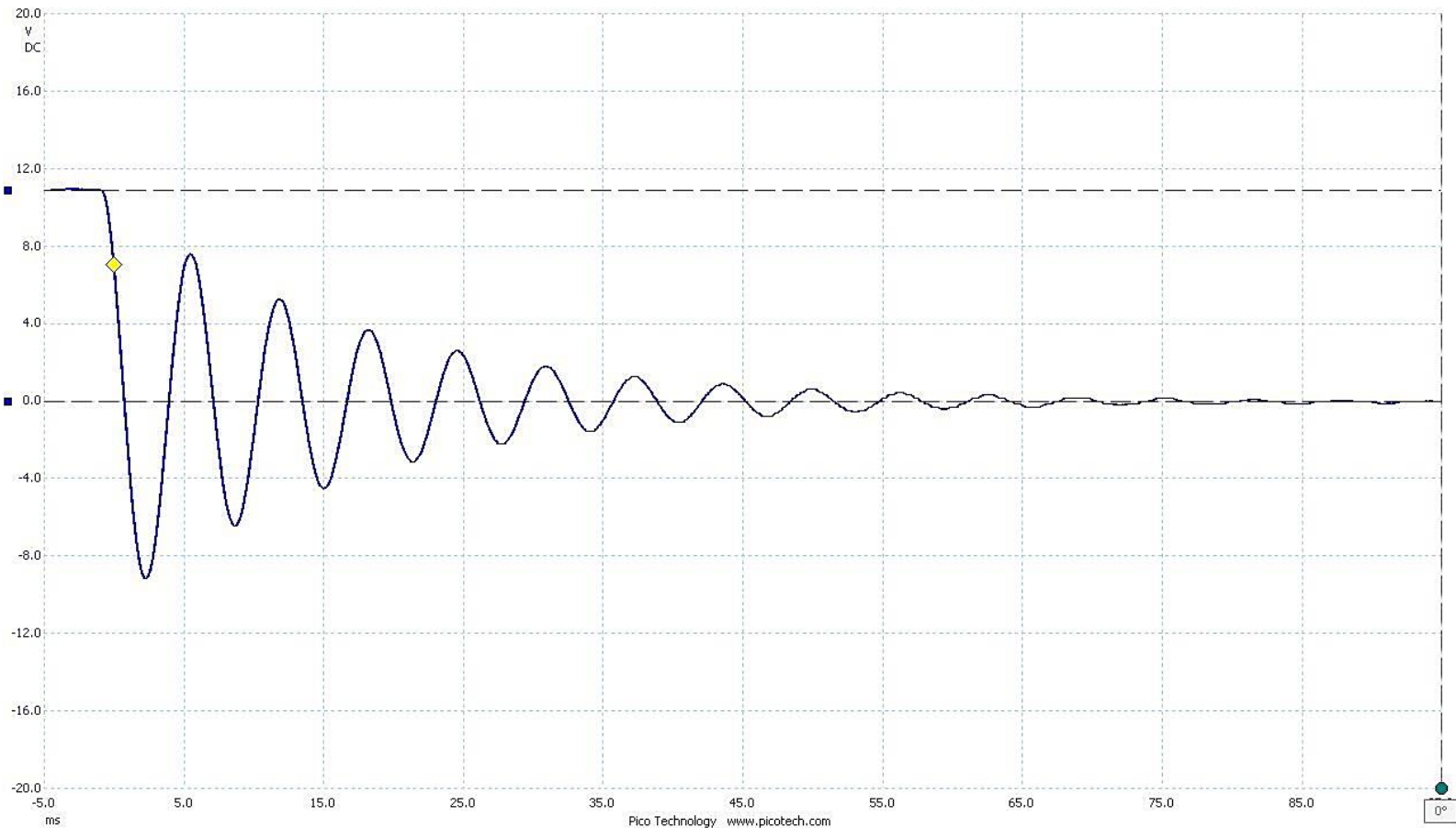


Figure 2. Capacitor: 1007 nF Inductor: 996 mH

The L-R-C Series Circuit

Damped harmonic oscillation:

$$q(t) = Ae^{-\beta t} \cos(\omega_1 t + \phi)$$

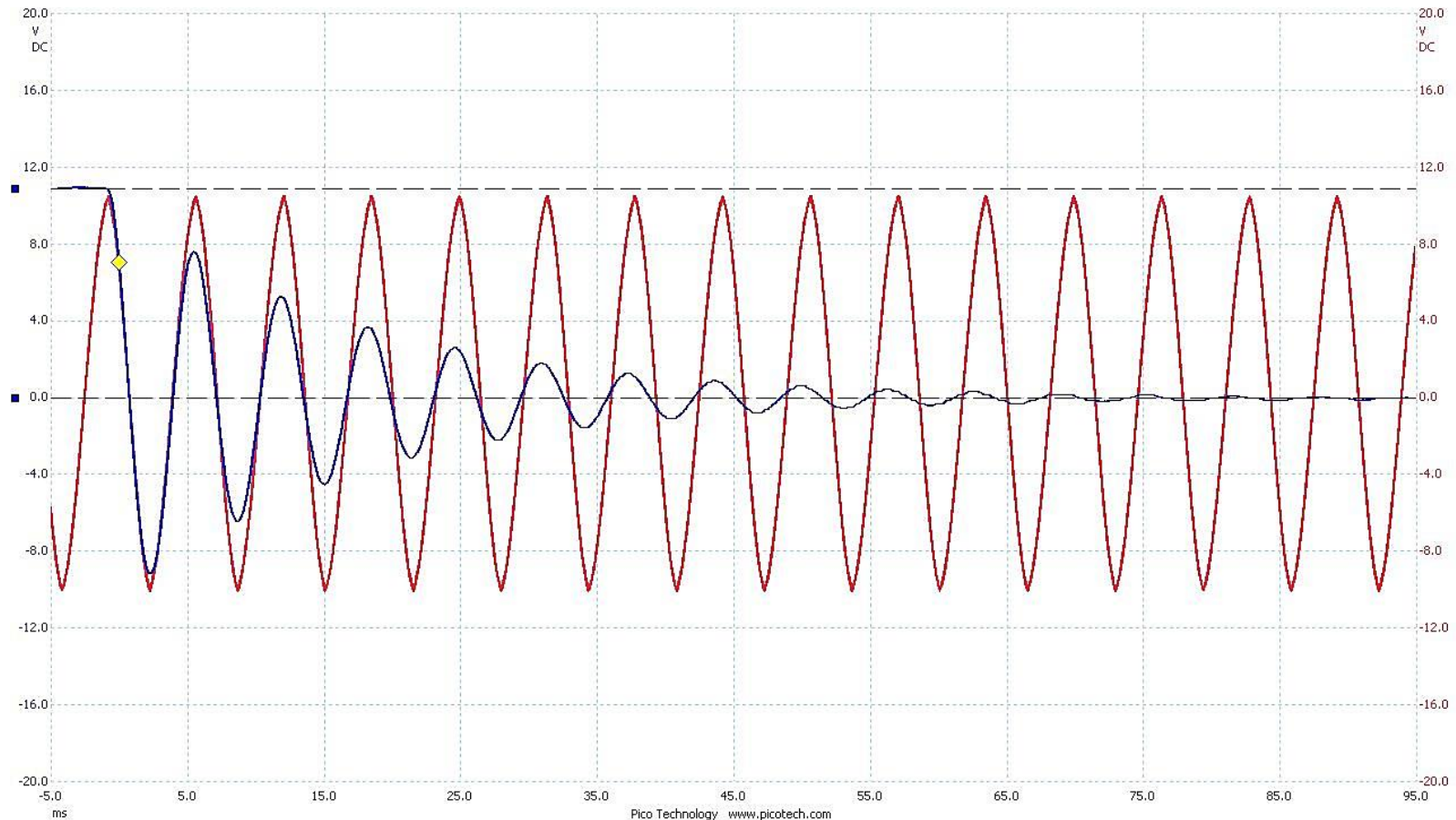


Figure 2. Capacitor: 1007 nF Inductor: 996 mH

The L-R-C Series Circuit

Damped harmonic oscillation:

$$q(t) = Ae^{-\beta t} \cos(\omega_1 t + \phi)$$

- *Energy in the capacitor:*

$$\begin{aligned} U_C &= \frac{1}{2C} q^2(t) \\ &= \frac{A^2}{2C} e^{-2\beta t} \cos^2(\omega_1 t + \phi) \end{aligned}$$

*The energy of the electric field oscillates according to a cosine-squared term, and the amplitude **decreases exponentially** with time.*

END

